

BANKURA UNIVERSITY

B. Sc. (HONOURS) FIRST SEMESTER EXAMINATIONS, 2021

Subject: Computer Science

Course ID: 11512

Course Title: Computer System Architecture

Full Marks: 25

Time: 1 Hr. 15 min

The figures in the margin indicate full marks

Answer all the questions.

UNIT I

1. Answer *any five* of the following questions: (1 × 5 = 5)

- a) Using 2's complement arithmetic subtract: 100 – 11000
- b) Represent the decimal number 8620 to binary
- c) Write down the truth table of XOR gate
- d) Why is cache memory used?
- e) What is multiplexer?
- f) What is PROM?
- g) What is register?
- h) Define instruction cycle.

UNIT II

2. Answer *any two* of the following questions: (5 × 2 = 10)

- a) Design S-R flip-flop
- b) Design a Half-subtractor
- c) Distinguish between RAM and ROM
- d) Discuss the importance of memory reference instructions in computer with examples.

UNIT III

3. Answer *any one* of the following questions: (10 × 1 = 10)

- a) Obtain the simplified expression of $F(w, x, y, z) = \sum (1, 4, 6, 7, 8, 9, 10, 11, 15)$. Implement a full-adder circuit using a decoder circuit and basic gates. (5 + 5)

- b) Discuss with a block diagram for Direct Memory Access transfer. Write short notes on different types of System Bus. (6 + 4)

XXXXXXXXXXXXXXXXXXXXXXX